

HINGA MUNA!!!



IEE1-(AC Circuits Part 2)

Review Materials for EE subject

AC Circuits Part 2


Three Phase Circuits / Systems



same parameters - same power factor

Balanced 3 ϕ Circuits/ Systems:


i. Wye (Star) Connected System

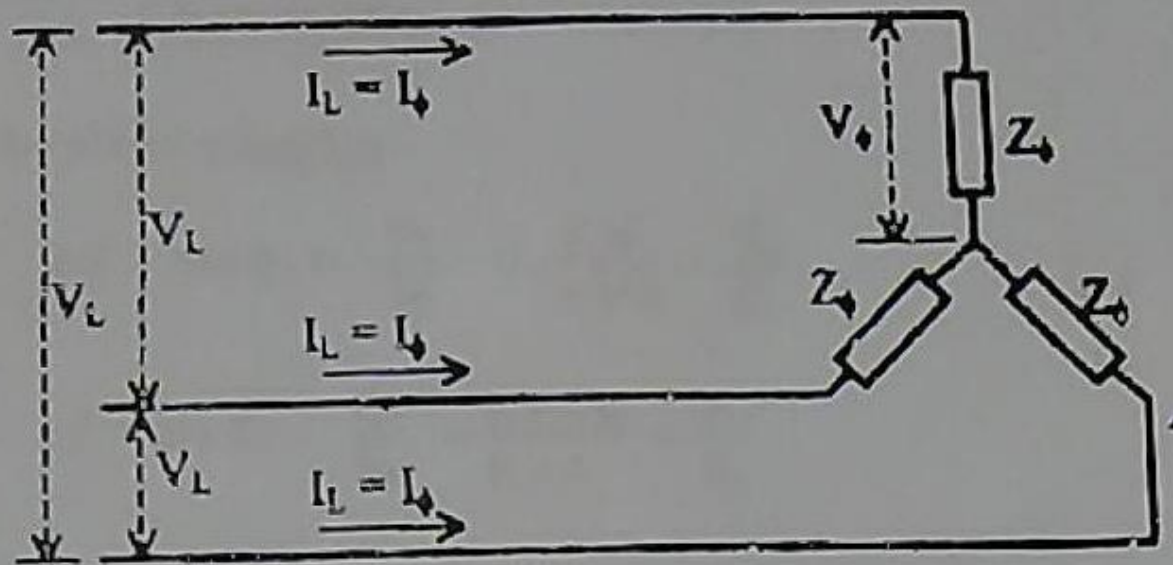

Relationships :

$$I_\phi = I_L \quad ; \quad V_\phi = \frac{V_L}{\sqrt{3}}$$

2 Delta (Mesh) Connected System:

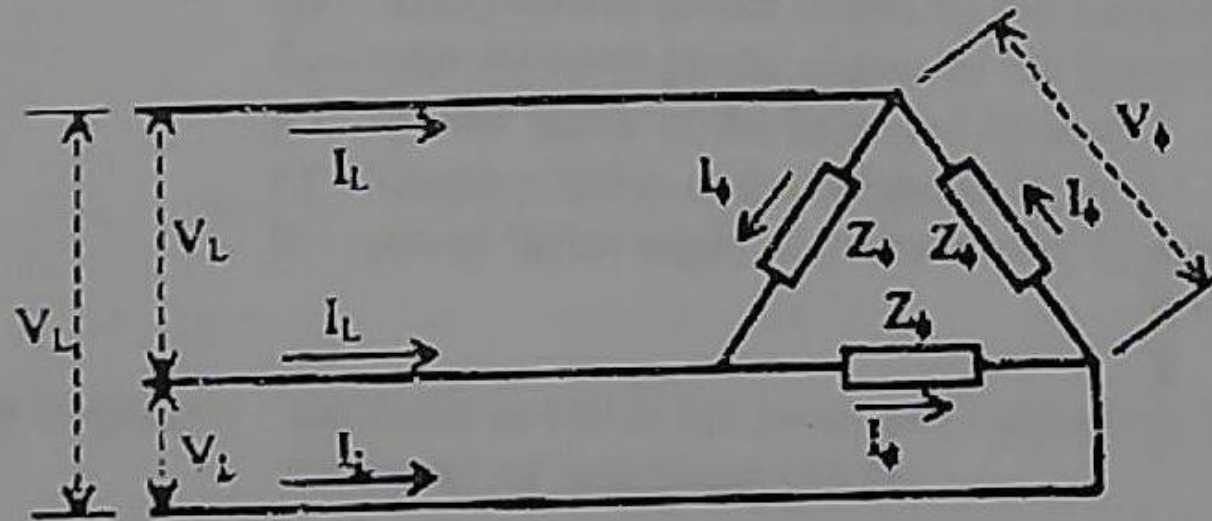

Relationships:

$$V_\phi = V_L$$

;

$$I_\phi = \frac{I_L}{\sqrt{3}}$$

where:

V_ϕ – phase voltage

I_ϕ – phase current

V_L – line voltage

I_L – line current



Power in Balanced 3 ϕ Circuits/Systems (Whether Wye or Delta connected)


$$P_T = \sqrt{3} V_L I_L (\text{p.f.}) = 3 V_{\phi} I_{\phi} (\text{p.f.}) = 3 I_{\phi}^2 R_{\phi} \text{ watts}$$

$$Q_T = \sqrt{3} V_L I_L (\text{r.f.}) = 3 V_{\phi} I_{\phi} (\text{r.f.}) = 3 I_{\phi}^2 X_{\phi} \text{ vars}$$


$$S_T = \sqrt{3} V_L I_L = 3 V_{\phi} I_{\phi} = 3 I_{\phi}^2 Z_{\phi} = \sqrt{P_T^2 + Q_T^2} \text{ va}$$



Power Triangle:

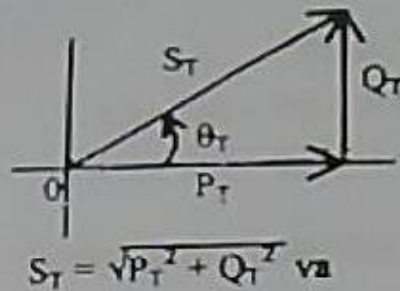

Impedance Triangle:

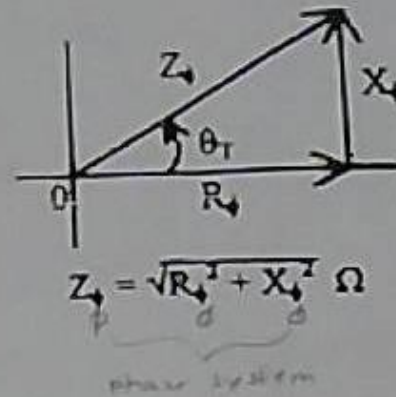

From the above triangles:

$$\text{p.f.} = \cos \theta_T = \frac{P_T}{S_T} = \frac{\text{KW}}{\text{KVA}} = \frac{R_L}{Z_L}$$

$$\text{r.f.} = \sin \theta_T = \frac{Q_T}{S_T} = \frac{\text{KVAR}}{\text{KVA}} = \frac{X_L}{Z_L}$$

$$\tan \theta_T = \frac{Q_T}{P_T} = \frac{\text{KVAR}}{\text{KW}} = \frac{X_L}{R_L}$$

where:

- P_T – total real power drawn by the balanced 3ϕ load
- Q_T – total reactive power drawn by the balanced 3ϕ load
- S_T – total apparent power drawn by the balanced 3ϕ load
- p.f. – power factor of the balanced 3ϕ load
- r.f. – reactive factor of the balanced 3ϕ load
- θ_T – power factor angle of the balanced 3ϕ load



Phase Sequence – the order in which the generated voltages in the phase windings of an alternator reach or attain their peak or maximum values.


a. Positive Phase Sequence

$ABC \rightarrow BCA \rightarrow CAB$


$AB - BC - CA \rightarrow BC - CA - AB \rightarrow CA - AB - BC$

$AN - BN - CN \rightarrow BN - CN - AN \rightarrow CN - AN - BN$


Examples of Vector Representations

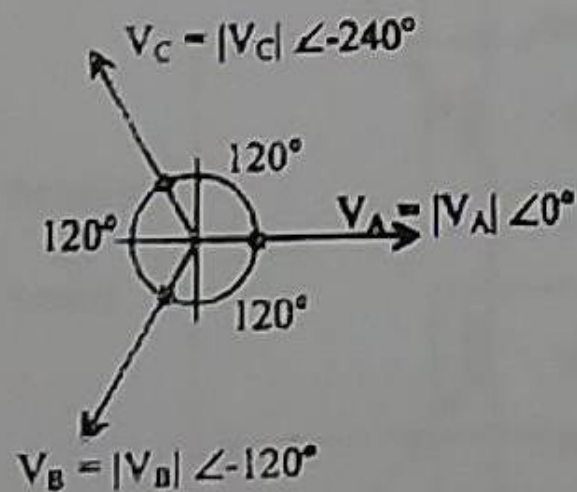

Sequence ABC

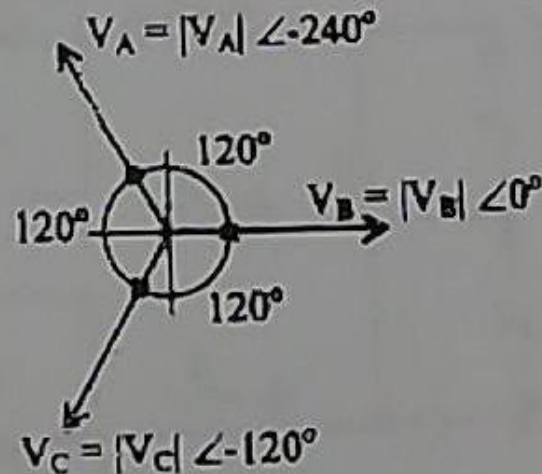

Sequence BCA

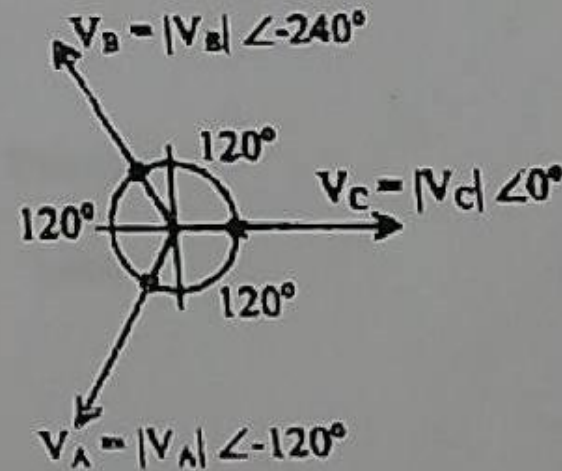

Sequence CAB




b. Negative Phase Sequence

$$ACB \rightarrow CBA \rightarrow BAC$$


$$AB - CA - BC \rightarrow CA - BC - AB \rightarrow BC - AB - CA$$

$$AN - CN - BN \rightarrow CN - BN - AN \rightarrow BN - AN - CN$$


Examples of Vector Representations

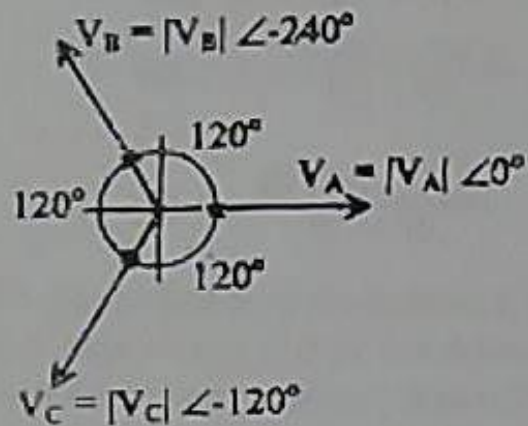

Sequence ACB

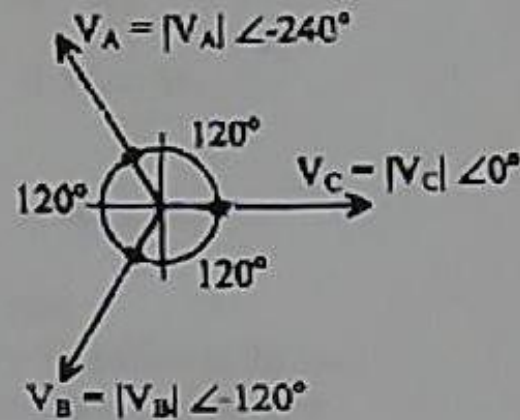

Sequence CBA

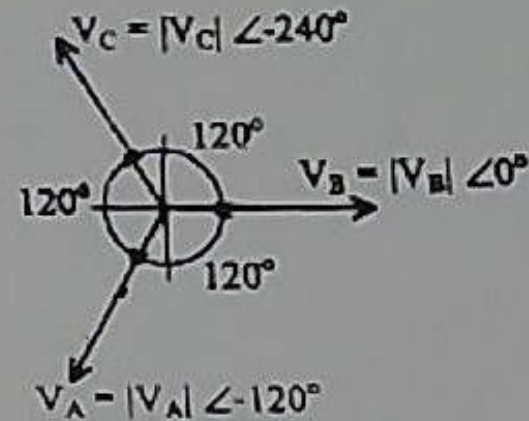

Sequence BAC

If the phase sequence is not given, assume a positive phase sequence. Three phase (3 ϕ) alternators are designed to operate with positive phase sequence voltages.






Power Measurements in three Phase (3ϕ) Systems

1. **One-wattmeter Method** – used to measure the total real power in a balanced three-phase system with a single wattmeter.

Methods employed:

- a. Potential – lead shift Method
- b. Artificial – neutral Method
- c. T Method
- d. Current-transformer Method

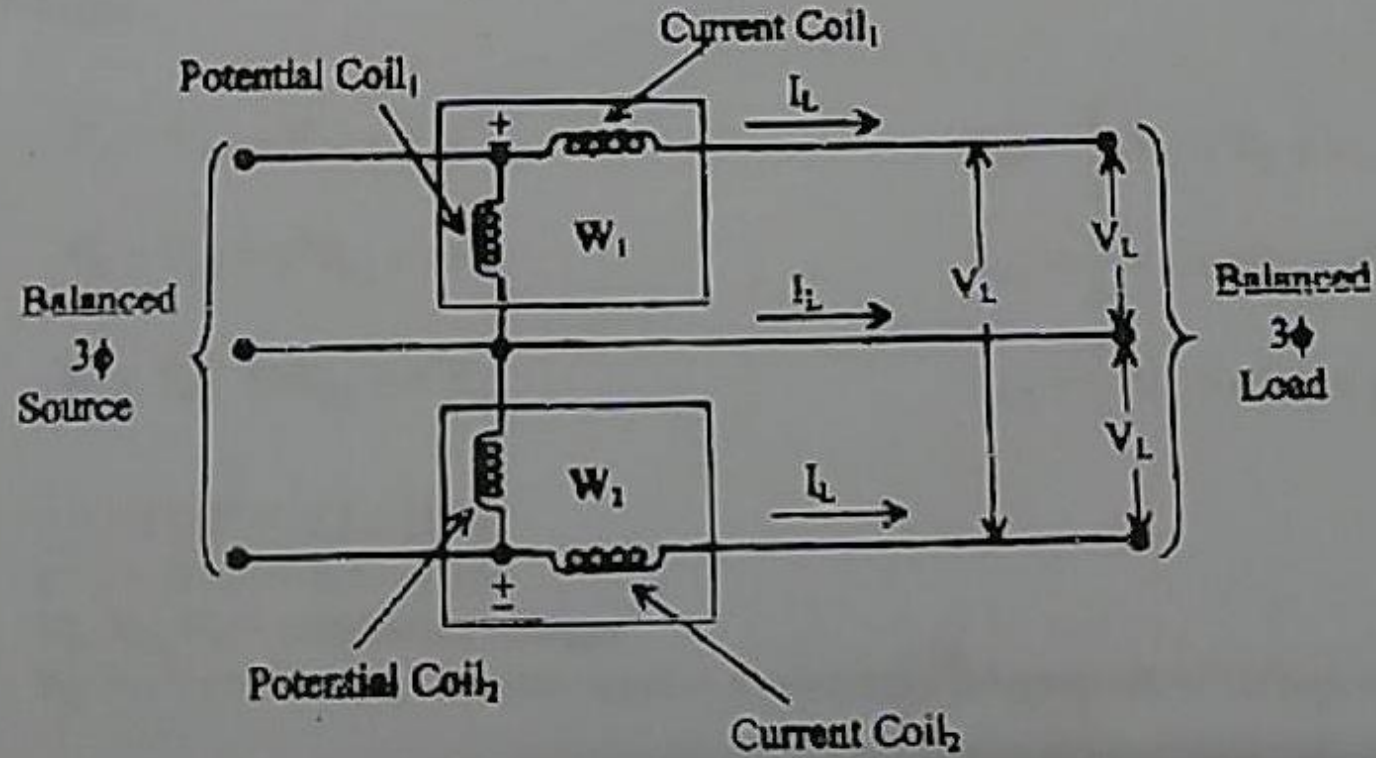2. **Two-wattmeter Method** – usually used to measure the real power being drawn by a three-phase (3ϕ), 3-wire system.



$$W_1 = V_L I_L \cos [30^\circ \pm \theta]$$

$$W_2 = V_L I_L \cos [30^\circ \mp \theta]$$

$$P_T = W_1 + W_2 \rightarrow \text{added algebraically}$$

$$Q_T = \sqrt{3} (W_1 - W_2), \quad \text{if } W_1 > W_2$$

$$Q_T = \sqrt{3} (W_2 - W_1), \quad \text{if } W_2 > W_1$$

$$\tan \theta = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2}, \quad \text{if } W_1 > W_2$$

$$\tan \theta = \frac{\sqrt{3} (W_2 - W_1)}{W_1 + W_2}, \quad \text{if } W_2 > W_1$$

where: θ = power factor of the balanced 3 ϕ load

P_T = total real or true power drawn by the balanced 3 ϕ load

Q_T = total reactive power drawn by the balanced 3 ϕ load

Notes:

1. At unity p.f., the two wattmeters have equal reading. That is $W_1 = W_2$
2. At 0.866 p.f., one wattmeter reading is twice the other
3. At 0.5 p.f., one wattmeter reads zero while the other registers the total circuit power
4. At less than 0.5 p.f., one wattmeter gives a negative reading and the other positive.



Symmetrical Components

Fortescue's Theorem: A set of n unbalanced related phasors may be resolved into n systems of balanced phasors called the **symmetrical components**.

For three-phase systems, we have:

- a. positive sequence component
- b. negative sequence component
- c. zero sequence component

For Voltages:

$$V_A = V_{A0} + V_{A1} + V_{A2}$$

$$V_B = V_{A0} + a^2 V_{A1} + a V_{A2}$$

$$V_C = V_{A0} + a V_{A1} + a^2 V_{A2}$$

$$V_{A0} = \frac{1}{3}(V_A + V_B + V_C)$$

$$V_{A1} = \frac{1}{3}(V_A + a V_B + a^2 V_C)$$

$$V_{A2} = \frac{1}{3}(V_A + a^2 V_B + a V_C)$$

where: $a = 1 \angle 120^\circ = -0.5 + j0.866$

$a^2 = 1 \angle 240^\circ = -0.5 - j0.866$

V_A, V_B, V_C = unbalanced voltages

V_0, V_1, V_2 = zero, positive and negative symmetrical components of voltage respectively



For Currents

$$I_A = I_{A0} + I_{A1} + I_{A2}$$

$$I_B = I_{A0} + a^2 I_{A1} + a I_{A2}$$

$$I_C = I_{A0} + a I_{A1} + a^2 I_{A2}$$

$$I_N = I_A + I_B + I_C$$

$$I_{A0} = \frac{1}{3} (I_A + I_B + I_C)$$

$$I_{A1} = \frac{1}{3} (I_A + a I_B + a^2 I_C)$$

$$I_{A2} = \frac{1}{3} (I_A + a^2 I_B + a I_C)$$

where: I_A, I_B, I_C = unbalanced currents

I_0, I_1, I_2 = zero, positive and negative symmetrical components of current respectively

I_N = neutral current



PART 2 – POLYPHASE SYSTEM

EXERCISES:

REE – Sept. 2013

1. Power in a three-phase delta system with balanced load is equal to
A. $\sqrt{3} V_L I_L$ (p.f.) B. $\sqrt{3} V_\phi I_\phi$ (p.f.) C. $3 V_\phi I_L$ (p.f.) D. $3 V_L I_L$ (p.f.)
2. In a balanced three-phase Y-connected system, the line voltage and the corresponding phase voltage are displaced from each other by _____.
A. 0° B. 30° C. 90° D. 120°
3. In balanced star (wye) connected system, the line voltage is _____.
A. 0.707 times the phase voltage B. 1.414 times the phase voltage
C. phasor sum of two phase voltages D. phasor difference of two phase voltages

REE – Sept. 2017

4. What is V_{BN} in this balanced three-phase in which $V_{AN} = 7200 \angle 20^\circ$ and $V_{CN} = 7200 \angle -100^\circ$?
A. $7200 \angle -80^\circ$ B. $7200 \angle 120^\circ$ C. $7200 \angle 90^\circ$ D. $7200 \angle 140^\circ$

REE – April 2002

5. Three 10-ohm resistors connected in wye are supplied from a balanced three phase source where phase a line voltage is given by $230 \sin 377t$. What is the phase a line current?
A. $13.28 \sin 377t$ B. $13.28 \sin(377t - 30^\circ)$
C. $23 \sin(377t - 30^\circ)$ D. $40 \sin(377t + 30^\circ)$



REE – April 2016

6. A balanced delta load of $3 + j4 \Omega$ per phase is connected to a balanced 110 v source. Find the line current
- A. 22 A B. 38.1 A C. 11 A D. 19.05 A

REE – Sept. 2011

7. A balanced three-phase 4,157 v rms source supplies a balanced three-phase delta-connected load of $38.4 + j28.8 \Omega$. Find the current in line A with V_{an} as reference
- A. $120 - j90$ A B. $120 + j90$ A C. $-120 + j90$ A D. $-120 - j90$ A

REE – Sept. 2017

8. Find the average power absorbed by a balanced three-phase load in an ABC circuit in which $V_{CB} = 208 \angle 15^\circ$ and $I_B = 3 \angle 110^\circ$?
- A. 1,080 W B. 624 W C. 358 W D. 620 W
9. A system consists of three equal resistors connected in delta and is fed from a balanced three-phase supply. How much power is reduced if one of the resistors is disconnected?
- A. 33% B. 50% C. 25% D. 0%

REE – April 2005

10. Three heater units each taking 1,500 watts are connected delta to a 120 volt three phase line. What is the resistance of each unit in ohms?
- A. 9.6 B. 5.4 C. 8.6 D. 7.5
11. The resistance between any two terminals of a balanced delta-connected load is 12 ohms. The resistance of each phase is _____
- A. 12 ohms B. 18 ohms C. 6 ohms D. 36 ohms





REE – Sept. 2013

12. A 240 v balanced 3 Φ source supplies a purely resistive impedance of 11.52 ohms per phase. What is the total power drawn if it is Y-connected?
- A. 5 kW B. 15 kW C. 20 kW D. 30 kW

REE – March 1998

13. Three impedances, $-j10$, $j10$ and 10Ω are wye connected. Determine the impedance of an equivalent delta.
- A. 12.5 , $j12.5$, -12.5Ω B. 10 , $j10$, $-j10\Omega$
C. $j8.5$, $j12.5$, 8Ω D. 5 , $5j$, $-j5\Omega$

REE – Sept. 2015 / Sept. 2016

14. Convert the delta connected impedances of $12\angle 36^\circ\Omega$ to balanced wye connected impedances.
- A. $3\angle 36^\circ\Omega$ B. $6\angle 36^\circ\Omega$ C. $4\angle 36^\circ\Omega$ D. $12\angle 36^\circ\Omega$
15. Three identical capacitances, each of $150\mu\text{F}$ are connected in star. The value of capacitance in each phase of the equivalent delta connected load would be _____.
- A. $150\mu\text{F}$ B. $450\mu\text{F}$ C. $50\mu\text{F}$ D. $300\mu\text{F}$

REE – Sept. 2007

16. A balanced three-phase, wye-connected load of 150 kw takes a leading current of 100 A, when the line is 2,400 v, 60 HZ. What is the capacitance per phase?
- A. 21 mF B. 21 μF C. 205 mF D. 205 μF

REE – April 2004

17. It is required to increase the power factor of a 750 KW three-phase balanced load from 70% lagging to 90% lagging. The line voltage is 6 900 volts, 60 Hz. Specify the capacitor required to increase the power factor of this wye-connected load in microfarad per phase.
- A. 20 45 B. 22 39 C. 18 58 D. 17 22

REE – May 2010

18. A balanced three-phase source serves three loads:

Load 1: 24 KW, 0.6 lagging p f

Load 2: 10 KW, unity p f

Load 3: 14 KVA, 0.8 leading p f

If the line voltage of the load is 208 v rms at 60 Hz, find the line current.

- A. 143 A B. 139 A C. 141 A D. 137 A
19. Two balanced loads are connected in parallel to a three phase 460-volt source. Load A is 90 kVA at a power factor of 0.6 lagging and load B is 25 kVA at unity power factor. What is the new power factor of the system?
- A. 0.74 lagging B. 0.74 leading C. 0.80 lagging D. 0.80 leading

REE – Sept. 2009

20. In two-wattmeter method of power measurement, the readings of the two wattmeters were 6,717 watts and 2,658 watts, respectively. Find the power factor.
- A. 0.90 B. 0.70 C. 0.60 D. 0.80

REE – April 2005

21. The total power consumed by a balanced 3 Φ load is 3,000 watts at 80% power factor. Two wattmeters W_A and W_B are connected to the line. What is the reading of W_A ?
- A. 2,150 watts B. 2,000 watts C. 1,500 watts D. 2,500 watts



REE – Sept. 2008

22. In a balanced three – phase 230 V circuit, the line current is 90 A. The power is measured by two – wattmeter method. If the power factor is 100% and the line current is the same, what is the reading on each wattmeter?
- A. 25.6 kW B. 30.4 kW C. 17.9 kW D. 20.7 kW

REE – Sept. 2016

23. The type of ac distribution system commonly used to supply both light and power is the
- A. open delta system
B. three-phase delta system
C. three-phase wye system with neutral wire
D. three-phase wye system without neutral wire

REE – Sept. 2015

24. For an unbalanced load which connection is suitable?
- A. 3 – wire open delta C. 3 – wire delta connection
B. 4 – wire wye connection D. 3 – wire wye connection

REE – Sept. 2009

25. A three-phase, wye-connected system with 240-v per phase is connected to three loads: 10 ohms, $18.79 + j6.84$ ohms, $9.83 - j6.88$ ohms to phases A, B, and C, respectively. Find the current in phase C.
- A. $1.74 + j19.92$ A B. $-1.74 + j19.92$ A C. $-1.74 - j19.92$ A D. $1.74 - j19.92$ A
26. A three-phase, four-wire system has the following unbalanced loads: $Z_a = 10 + j10\Omega$, $Z_b = 13 - j2\Omega$, $Z_c = 7.5 + j10\Omega$. Determine the total power delivered to the load if the line voltage is 208 V.
- A. 4.48 kW B. 1.48 kW C. 2.49 kW D. 2.90 kW





REE – April 2005

27. A 3-phase 4-wire system has the following unbalanced loads $Z_1 = 10 + j5 \Omega$, $Z_2 = 8 + j4 \Omega$, and $Z_3 = 20 + j0 \Omega$. The line to neutral voltage of the system is 120 volts. What is the reading of the wattmeter in watts in Z_3 ?
- A. 900 B. 720 C. 1,000 D. 1,050

REE – March 1998

28. The three unbalanced currents are $I_a = 10 \text{ cis}(-30^\circ)$, $I_b = 0$, $I_c = 10 \text{ cis } 150^\circ$. Find the negative sequence of phase A current.
- A. $8.66 \text{ cis } 30^\circ \text{ A}$ B. $5.77 \text{ cis } (-60^\circ) \text{ A}$ C. -5.77 A D. 5.77 A

REE – Oct. 1998

29. The load of a wye connected transformer are: $I_a = 10 \text{ cis}(-30^\circ)$, $I_b = 12 \text{ cis } 215^\circ$, $I_c = 15 \text{ cis } 82^\circ$. What is the neutral current?
- A. $1.04 \text{ cis } 72.8^\circ$ B. $0.92 \text{ cis } 62.5^\circ$ C. $2.21 \text{ cis } (-30^\circ)$ D. $3.11 \text{ cis } 72.8^\circ$

REE – Sept. 2007

30. For the following phase currents $I_a = 34.64$, $I_b = -10 - j17.32$, $I_c = -10 + j17.32$. What is the positive sequence for phase c?
- A. $12.44 - j21.55$ B. $12.44 + j21.55$ C. $-12.44 + j21.55$ D. $-12.44 - j21.55$

31. A wye-connected, three phase system has the following sequence components of current:

Zero sequence current = $12.5 \text{ cis } 30^\circ$

Positive sequence current = $28 \text{ cis } (-45^\circ)$

Negative sequence current = $20 \text{ cis } (-32^\circ)$

Determine the current flowing in the neutral wire.

- A. $4.17 \text{ cis } 30^\circ$ B. $37.5 \text{ cis } 30^\circ$ C. $35.7 \text{ cis } (-60^\circ)$ D. $22.5 \text{ cis } 10^\circ$

REE – April 2007

32. Given the following sets of symmetrical components, determine the phase current for phase B

$I_{a0} = 1 \text{ at } 75^\circ$ $I_{a1} = 1 \text{ at } 15^\circ$ $I_{a2} = 1 \text{ at } -45^\circ$

- A. $0.259 + j0.966$ B. $0.516 + j1.931$ C. $1.932 + j0.518$ D. $1.414 + j1.414$

REE – Sept. 2006 / April 2017

33. One conductor of a three-phase line is open. The current flowing to the delta-connected load through line a is 20 A. With the current in line a as reference and assuming that line c is open, what is the negative sequence current of phase a?

- A. $10 + j5.78$ B. $10 - j5.78$ C. $j11.55$ D. $-10 + j5.78$

